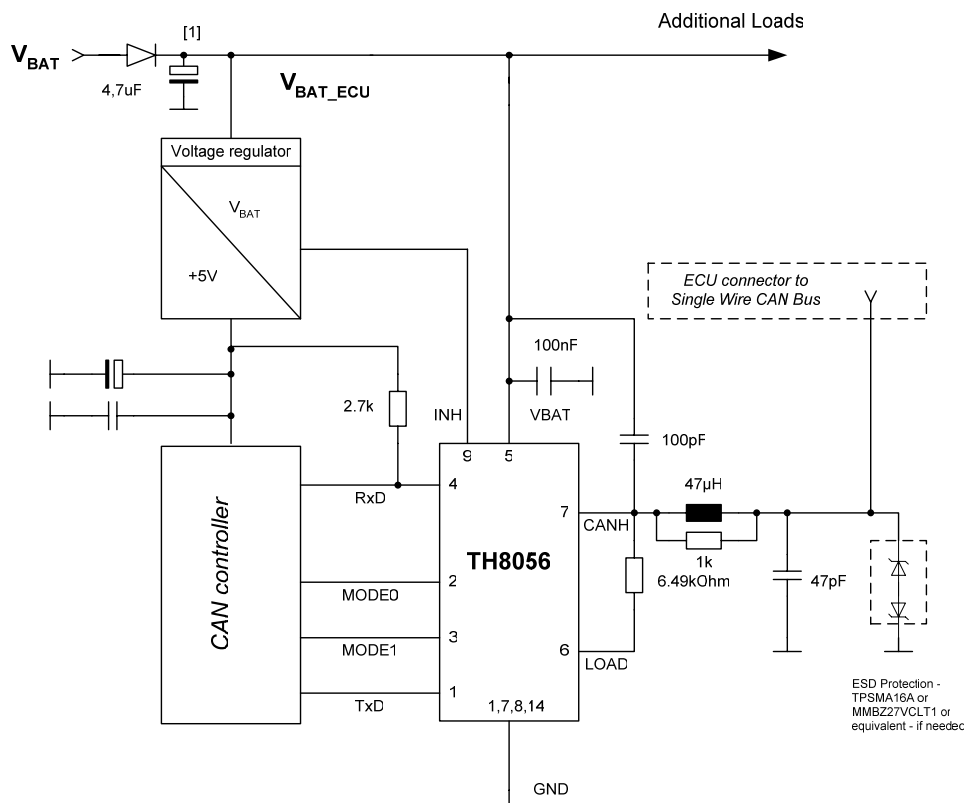


### 1 Scope

This document describes application hints for using the Melexis Enhanced Single Wire CAN Transceiver TH8056 by using a reservoir capacitor > 500uF on pin Vbat.

**ATTENTION!** This application note is only valid if the used application circuitry differs from the standard application circuitry according to Single Wire CAN Physical Layer Specification GMW3089 V2.3 section 3.12.1 (see Figure 1). The GMLAN Device Test Specification GME6718GS will always be passed with the standard application circuitry. The following hints are only necessary for special applications which are using an additional reservoir capacitor > 500uF on pin Vbat.

### 2 Recommended application circuitry




[1] recommended capacitance at VBAT\_ECU > 1uF (immunity to ISO7637/1 test pulses)

**Figure 1 Application circuitry according GMW3089 V2.3**

This recommended application circuitry of the TH8056 fulfills completely the GMLAN Device Test Specification GME6718GS Rev. 1.7.
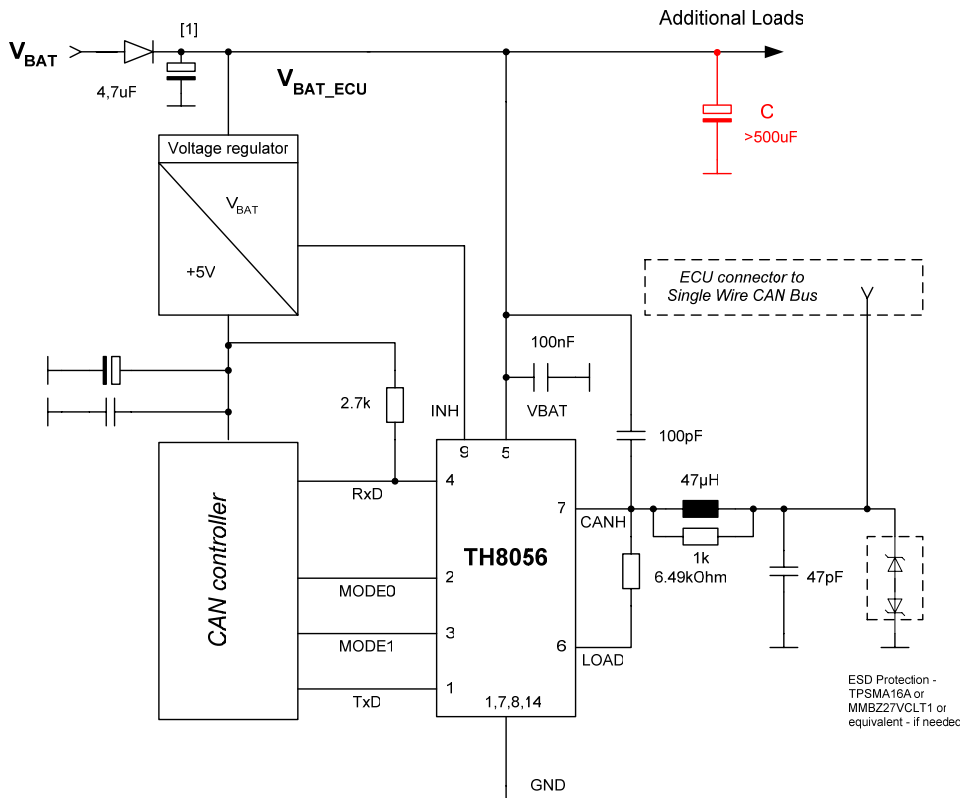
### 3 Special application circuitry including a reservoir capacitor > 500µF

The following application circuitry uses an additional reservoir capacitor >500µF on the pin Vbat, which differs from the recommended application circuitry of the Single Wire CAN Physical Layer Specification GMW3089 V2.3 section 3.12.1.



[1] recommended capacitance at VBAT\_ECU > 1uF (immunity to ISO7637/1 test pulses)

**Figure 2 Special application circuitry**

This special application circuitry of the TH8056 fulfills the GMLAN Device Test Specification GME6718GS Rev 1.7 **except** section 2.11.6 (Bus short to battery).

The test described in section 2.11.6 will not be fulfilled under the following conditions:


- Using of reservoir capacitors greater than 500µF
- A very short rise time of the voltage at pin CANH
- No current limitation of the power supply available

To fulfill the GMLAN Device Test Specification GME6718GS Rev 1.7 without any exceptions a small change of the external components is necessary.

There are three different solutions possible:

- Adding reverse protection diode between reservoir capacitor and TH8056 (see 3.1)
- Adding a series resistor > 510Ω to the reservoir capacitor (see 3.2)
- Adding a series resistor > 510Ω in parallel with a diode to the reservoir capacitor (see 3.3)
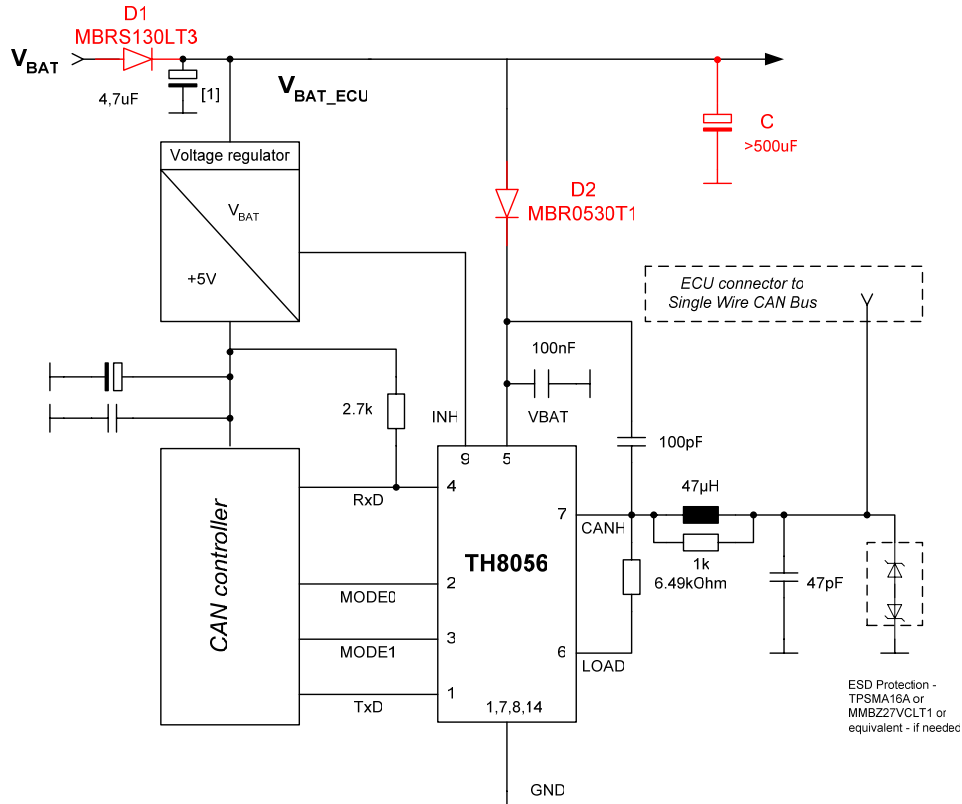
### 3.1 Solution 1 - Adding reverse protection diode D between reservoir capacitor and TH8056




[1] recommended capacitance at VBAT\_ECU > 1uF (immunity to ISO7637/1 test pulses)

**Figure 3 Solution 1**

The module will be powered from the battery through the first reverse polarity protection diode. The capacitor will be charged to battery voltage. Only the transceiver will be powered through the second reverse polarity diode with the additional voltage drop. To be compliant with GM3089, the added diode D2 should provide a low forward voltage drop. Also the original reverse protection diode D1 should be replaced by a schottky diode.
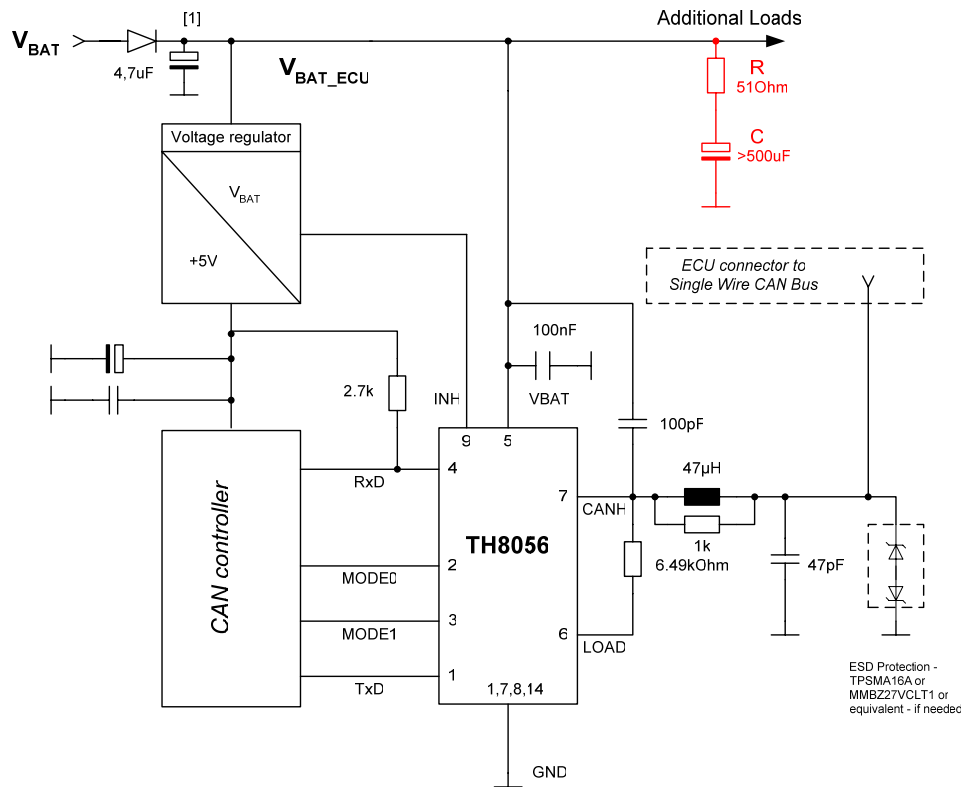
### 3.2 Solution 2 - Adding a series resistor $R > 510\Omega$ to the reservoir capacitor




[1] recommended capacitance at VBAT\_ECU > 1uF (immunity to ISO7637/1 test pulses)

**Figure 4 Solution 2**

In normal application mode the 510Ohm series resistor  $R$  has no influence to the module behaviour (in accordance to GMW3089). The module will be powered from the battery through the reverse polarity protection diode. The capacitor  $C$  will be charged to battery voltage.

For the cranking pulse the module will be powered by the capacitor  $C$ . The current consumption of the transceiver is approximately 5mA with no bus traffic during cranking. Current consumption of the other components is estimated at approximately 50mA and a voltage drop caused by the resistor  $R$  is 2.5V. This has an influence on the available time of the connected microcontroller to save contents in an EEPROM or other time critical activities. This limitation can be improved by increasing the value of the capacitor  $C$ .
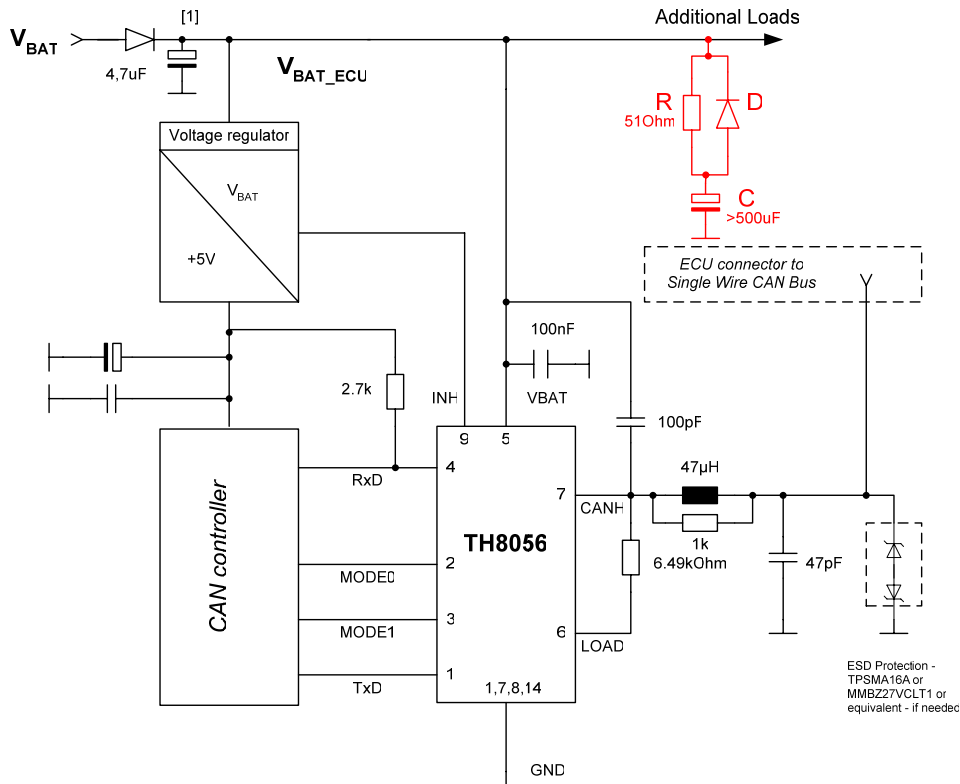
### 3.3 Solution 3 - Adding a series resistor $R > 510\Omega$ in parallel with a diode $D$ to the reservoir capacitor



[1] recommended capacitance at VBAT\_ECU > 1uF (immunity to ISO7637/1 test pulses)

**Figure 5 Solution 3**

In normal application mode the 510 Ohm series resistor has no influence to the module behaviour (in accordance to GMW3089). The module will be powered from the battery through the reverse polarity protection diode. The capacitor will be charged to battery voltage. In case of cranking pulse the module will be powered by the capacitor.

The voltage drop via the resistor caused by the current consumption of the module will be clamped to 0.4 to 1.0 V due to the forward biased diode. In this case minimal 10% of the available voltage margin is lost. The recommendation is that the added diode should be the same as the reverse polarity diode.

## **4 Disclaimer**

Devices sold by Melexis are covered by the warranty and patent indemnification provisions appearing in its Term of Sale. Melexis makes no warranty, express, statutory, implied, or by description regarding the information set forth herein or regarding the freedom of the described devices from patent infringement. Melexis reserves the right to change specifications and prices at any time and without notice. Therefore, prior to designing this product into a system, it is necessary to check with Melexis for current information. This product is intended for use in normal commercial applications. Applications requiring extended temperature range, unusual environmental requirements, or high reliability applications, such as military, medical life-support or life-sustaining equipment are specifically not recommended without additional processing by Melexis for each application.

The information furnished by Melexis is believed to be correct and accurate. However, Melexis shall not be liable to recipient or any third party for any damages, including but not limited to personal injury, property damage, loss of profits, loss of use, interrupt of business or indirect, special incidental or consequential damages, of any kind, in connection with or arising out of the furnishing, performance or use of the technical data herein. No obligation or liability to recipient or any third party shall arise or flow out of Melexis' rendering of technical or other services.

© 2002 Melexis NV. All rights reserved.

---

For the latest version of this document. Go to our website at  
[www.melexis.com](http://www.melexis.com)

Or for additional information contact Melexis Direct:

Europe and Japan:  
Phone: +32 1367 0495  
E-mail: [sales\\_europe@melexis.com](mailto:sales_europe@melexis.com)

All other locations:  
Phone: +1 603 223 2362  
E-mail: [sales\\_usa@melexis.com](mailto:sales_usa@melexis.com)

ISO/TS16949 and ISO14001 Certified